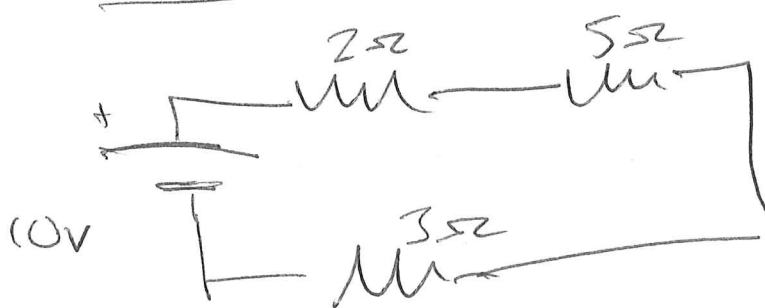


6

Solutions: Circuit practice worksheet



- Determine current, I , through the battery.
- Determine the voltage across the 3Ω resistor.

Step 1: Determine the total resistance of the circuit. note: these resistors are connected in series.

$$R_{net} = R_1 + R_2 + R_3$$

$$R_{net} = 2\Omega + 5\Omega + 3\Omega = 10\Omega$$


Step 2: Use the total, system resistance to calculate the total, system current.

$$V = IR \quad \frac{V}{R} = I \quad \left[\frac{10V}{10\Omega} = 1 \text{ amp} \right] = \text{Answer} = 1$$

Step 3: Use that current to determine voltage across 3Ω resistor

$$V = IR$$
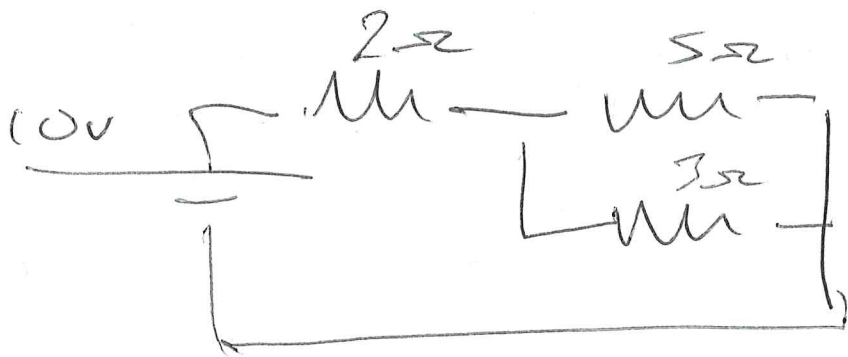
$$V = (1 \text{ amp})(3\Omega) = 3 \text{ volts}$$



- Determine voltage across 2Ω resistor.
- Determine current through the 3Ω.

① Determine total resistance of circuit. note: $5\Omega + 3\Omega$ resistors are in parallel.

$$\frac{1}{R_{net}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$\frac{1}{R_{net}} = \frac{1}{5} + \frac{1}{3} = \frac{3}{15} + \frac{5}{15} = \frac{8}{15} = \frac{1}{R_{net}}$$

$$\therefore R_{net} = \frac{15}{8} = 1.875\Omega$$

this combination of resistors acts like a single, 1.87Ω resistor

$$2\Omega + 1.875\Omega = 3.875\Omega \text{ total}$$


② Determine ^{total} current.

$$V = IR \quad \rightarrow \quad \frac{V}{R} = I = \frac{10V}{3.875\Omega} = 2.58 \text{ amperes}$$


③ Determine voltage drop across 2Ω resistor

$$V = IR, \quad V = (2.58A)(2\Omega) = 5.16 \text{ volts}$$

Continued next page

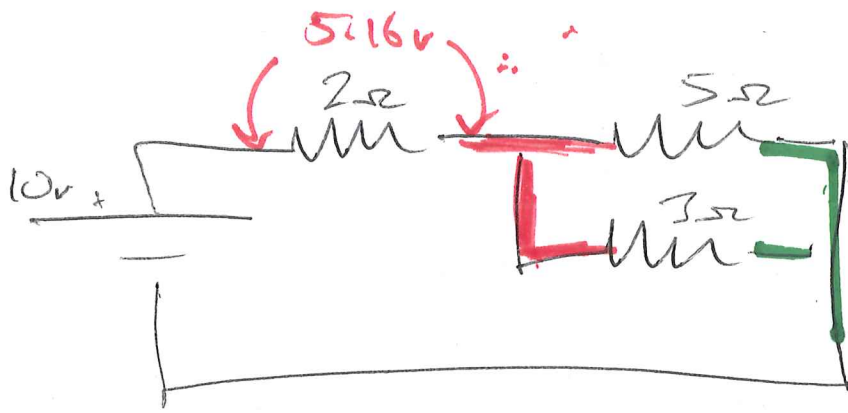

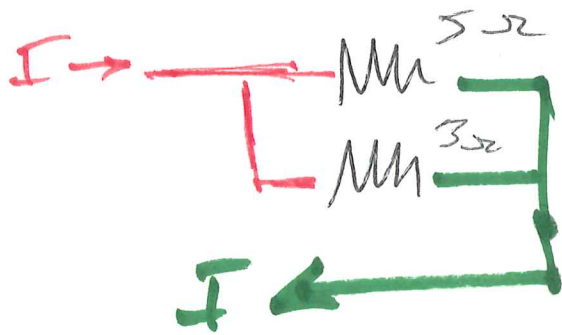- note: since the voltage drops by 5.16 volts across the 2Ω resistor, the voltage must drop by 4.84 volts across the next two resistors in parallel




$$\therefore V = IR$$

$$\frac{V}{R} = I \therefore \frac{4.84 \text{ V}}{3.5 \Omega} = \underline{1.61 \text{ amperes}}$$

Current through 3Ω

Done ☺

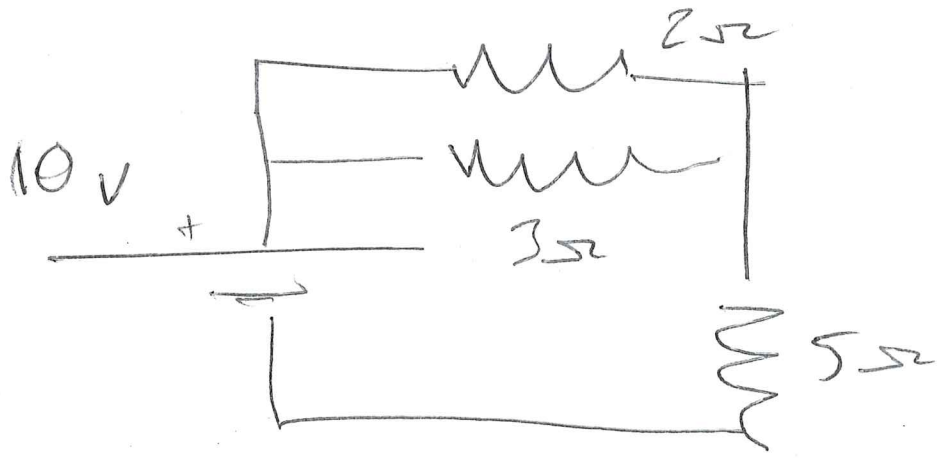

Determine
voltage across
5Ω resistor

Step 1: Determine resistance of entire circuit.
- first, determine resistance of the 2Ω + 3Ω in parallel.

$$\frac{1}{2} + \frac{1}{3} = \frac{1}{R_{\text{net}}} = \frac{3}{6} + \frac{2}{6} = \left[\frac{5}{6} = \frac{1}{R_{\text{net}}} \right]$$

now add 5Ω + 1.2Ω = 6.2Ω ∴ $R_{\text{net}} = \frac{6}{5} = 1.2\Omega$

total R = \rightarrow

Step 2

now: Determine total current in circuit

$$V = IR \therefore \frac{V}{R} = I \therefore \frac{10V}{6.2\Omega} = \underline{1.6 \text{ amps}}$$

Step 3: to determine voltage across the 5Ω resistor.

$$V = IR \therefore V = (1.6A)(5\Omega) = \underline{8.06 \text{ volts}}$$

done