

30. (II) Determine the magnitudes and directions of the currents in each resistor shown in Fig. 19-48. The batteries have emfs of $\mathcal{E}_1 = 9.0 \text{ V}$ and $\mathcal{E}_2 = 12.0 \text{ V}$ and the resistors have values of $R_1 = 25 \Omega$, $R_2 = 18 \Omega$, and $R_3 = 35 \Omega$.

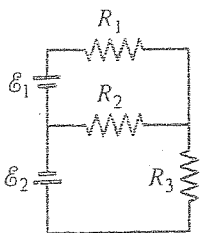


FIGURE 19-48
Problems 29 and 30.

30. (II) Repeat Problem 29, assuming each battery has internal resistance $r = 1.0 \Omega$.
31. (II) Calculate the currents in each resistor of Fig. 19-49.

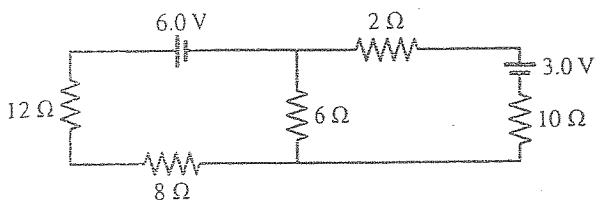


FIGURE 19-49 Problem 31.

32. (III) (a) Determine the currents I_1 , I_2 , and I_3 in Fig. 19-50. Assume the internal resistance of each battery is $r = 1.0 \Omega$. (b) What is the terminal voltage of the 6.0-V battery?

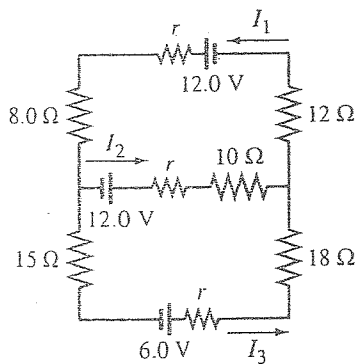


FIGURE 19-50
Problems 32 and 33.

33. (III) What would the current I_1 be in Fig. 19-50 if the 12- Ω resistor is shorted out? Let $r = 1.0 \Omega$.

19-4 Emfs Combined, Battery Charging

34. (II) Suppose two batteries, with unequal emfs of 2.00 V and 3.00 V, are connected as shown in Fig. 19-51. If each internal resistance is $r = 0.100 \Omega$, and $R = 4.00 \Omega$, what is the voltage across the resistor R ?

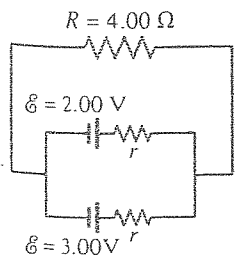


FIGURE 19-51
Problem 34.

ted to
has

24. (II) Determine the terminal voltage of each battery in Fig. 19-44.

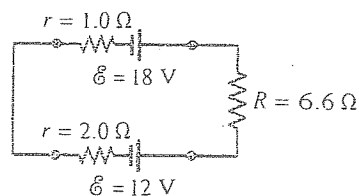


FIGURE 19-44 Problem 24.

25. (II) (a) What is the potential difference between points a and d in Fig. 19-45 (same circuit as Fig. 19-13, Example 19-8), and (b) what is the terminal voltage of each battery?

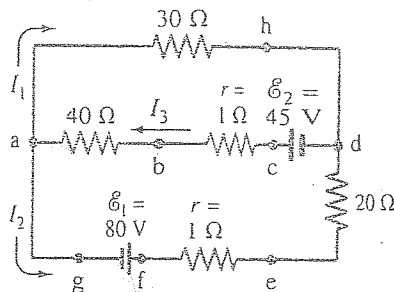


FIGURE 19-45 Problem 25.

26. (II) For the circuit shown in Fig. 19-46, find the potential difference between points a and b. Each resistor has $R = 75 \Omega$ and each battery is 1.5 V.

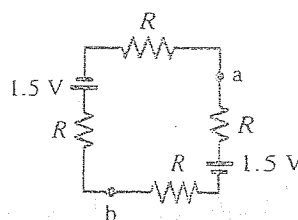


FIGURE 19-46 Problem 26.

27. (II) Determine the magnitudes and directions of the currents through R_1 and R_2 in Fig. 19-47.

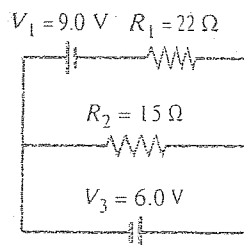


FIGURE 19-47 Problems 27 and 28.

28. (II) Repeat Problem 27, now assuming that each battery has an internal resistance $r = 1.2 \Omega$.

battery
opens
stors,
the
S is
(d) If
minal
tance
minal


d in
th a
num
that

* and
* the

*
*
*

MATRIX operations w/ TI calculator

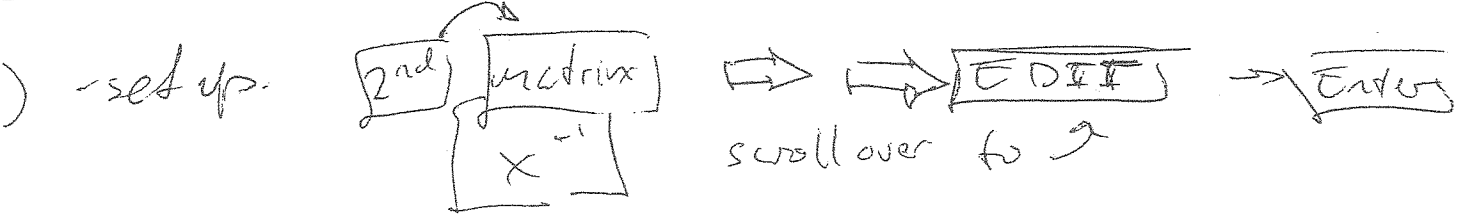- 1) set up matrix.
- 2) perform operations on matrix.




2) enter in size of matrix 3 x 4 in this case


and enter in values for each term*

$$\begin{cases}
 I_1 + I_2 + I_3 = \dots \\
 I_1 \quad I_2 \quad I_3 = \dots \\
 I_1 \quad I_2 \quad I_3 = \dots
 \end{cases}$$

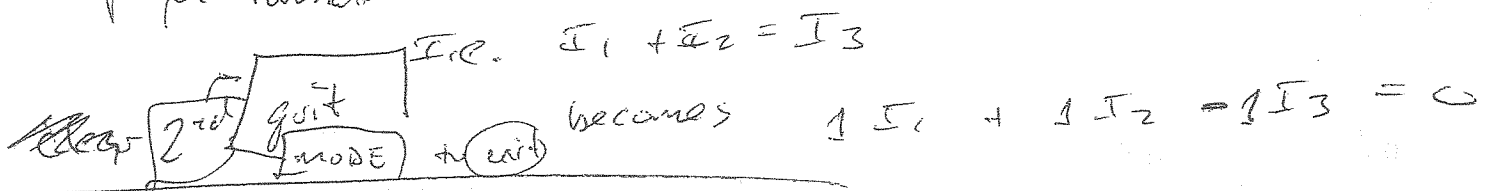* requires rewriting all equations into proper format



perform mathematical operations

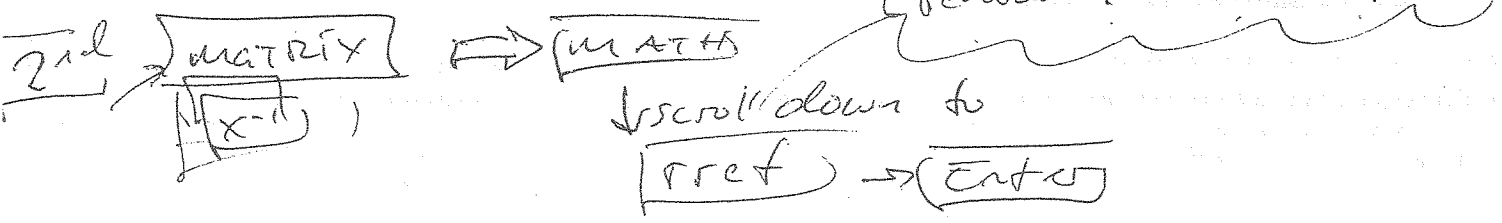

now the TI wants you to select the matrices to do math on.

